



Εθνικό Μετσόβιο Πολυτεχνείο
Σχολή Ηλεκτρολόγων Μηχανικών και Μηχανικών Υπολογιστών

Αναφορά 3ου εργαστηρίου
“Ψηφιακά Συστήματα VLSI”

ΟΝΟΜΑΤΕΠΩΝΥΜΑ	Χαλβατζόγλου Ιωάννα (ΑΜ: el21906) Αϊφαντή Ελισάβετ (ΑΜ: el22821)
ΟΜΑΔΑ	Ομάδα 13
ΔΙΔΑΣΚΟΝΤΕΣ	Κ.Πεκμεστζή Δ.Σούντρης Η. Παπαλάμπρου

MAC Unit:

❖ VHDL code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.std_logic_unsigned.ALL;

-- Multiplier Accumulator unit
entity MAC is
  generic (
    coeff_width: integer := 8;
    data_width : integer := 8;
    maximum_vector_length : integer := 19 -- coeff_width + data_width + log2(tap number: 8)
  );
  Port (
    clk : in std_logic;
    rom_out : in std_logic_vector (coeff_width-1 downto 0);
    ram_out : in std_logic_vector (data_width-1 downto 0);
    mac_init, valid_out : in std_logic;
    y_out : out std_logic_vector (maximum_vector_length - 1 downto 0)
  );
end MAC;

architecture Behavioral of MAC is
  signal feedback : std_logic_vector (maximum_vector_length - 1 downto 0) := (others => '0');
begin

  -- 2 cycle LATENCY per accumulation
  -- 1 cycle read from rom and ram
  -- 1 cycle to multiply and add

  process(clk)
  begin
    if (clk'event and clk = '1') then
      if mac_init = '1' then
        feedback <= (others => '0');
        feedback(coeff_width + data_width - 1 downto 0) <= rom_out * ram_out; -- begin next
accumulation
      else
        feedback <= feedback + rom_out * ram_out;
      end if;

      if valid_out = '1' then
        y_out <= feedback;
      end if;
    end if;
  end process;
end Behavioral;
```

```

    end if;
end process;

```

```

end Behavioral;

```

ROM:

❖ VHDL code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_unsigned.all;

entity mlab_rom is
    generic (
        coeff_width : integer :=8                --- width of coefficients
    )
    Port ( clk : in  STD_LOGIC;
          en : in  STD_LOGIC;                    --- operation enable
          addr : in  STD_LOGIC_VECTOR (2 downto 0);    -- memory address
          rom_out : out STD_LOGIC_VECTOR (coeff_width-1 downto 0));    -- output data
end mlab_rom;

architecture Behavioral of mlab_rom is

    type rom_type is array (7 downto 0) of std_logic_vector (coeff_width-1 downto 0);
    signal rom : rom_type:= ("00001000", "00000111", "00000110", "00000101", "00000100",
    "00000011", "00000010",
    "00000001");                                -- initialization of rom with user
    data

    signal rdata : std_logic_vector(coeff_width-1 downto 0) := (others => '0');
begin

    rdata <= rom(conv_integer(addr));

    process (clk)
    begin
        if (clk'event and clk = '1') then
            if (en = '1') then
                rom_out <= rdata;
            end if;
        end if;
    end process;
end Behavioral;

```

RAM:

❖ VHDL code

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ram is
    generic (
        data_width : integer :=8                --- width of data (bits)
    );
    port (clk : in std_logic;
          rst : in std_logic;
          we : in std_logic;                    --- memory write enable
          en : in std_logic;                    --- operation enable
          addr : in std_logic_vector(2 downto 0);    -- memory address
          di : in std_logic_vector(data_width-1 downto 0);    -- input data
          do : out std_logic_vector(data_width-1 downto 0));    -- output data
end ram;

architecture Behavioral of ram is

    type ram_type is array (7 downto 0) of std_logic_vector (data_width-1 downto 0);
    signal RAM : ram_type := (others => (others => '0'));    -- initialize at 0

begin
    process (clk, rst)
    begin
        if rst = '1' then
            RAM <= (others => (others => '0'));    -- reset to 0
        else
            if clk'event and clk = '1' then
                if en = '1' then
                    if we = '1' then                -- write operation
                        RAM(7 downto 1) <= RAM(6 downto 0);
                        RAM(conv_integer(addr)) <= di;
                        do <= di;
                    else                                -- read operation
                        do <= RAM(conv_integer(addr));
                    end if;
                end if;
            end if;
        end if;
    end process;

end Behavioral;
```

Control Unit:

❖ VHDL code

```
library IEEE;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.ALL;

entity control_unit is
  Port (
    clk      : in std_logic;
    rst      : in std_logic;
    valid_in  : in std_logic;
    rom_address : out std_logic_vector(2 downto 0);
    ram_address : out std_logic_vector(2 downto 0);
    mac_init   : out std_logic;
    we        : out std_logic;
    valid_out  : out std_logic
  );
end control_unit;

architecture Behavioral of control_unit is

  signal counter : std_logic_vector(2 downto 0) := (others => '0');
  signal temp_valid_out : std_logic_vector(8 downto 0) := (others => '0');

begin

  process(clk)
  begin
    if rising_edge(clk) then

      -- RESET
      if rst = '1' then
        counter <= (others => '0');
        temp_valid_out <= (others => '0');
        mac_init <= '1';
        we <= '0';

      else

        -- MAC init & write enable
        if counter = "000" then
          mac_init <= '1';
          we <= valid_in;
        else
          mac_init <= '0';
        end if;
      end if;
    end if;
  end process;

end Behavioral;
```

```

        we <= '0';
    end if;

    -- addresses
    rom_address <= counter;
    ram_address <= counter;

    -- counter
    if not (valid_in = '0' and counter = "000") then
        counter <= counter + 1;
    end if;

    -- delay 9 clk cycles
    temp_valid_out(0) <= valid_in;
    temp_valid_out(8 downto 1) <= temp_valid_out(7 downto 0);
    valid_out <= temp_valid_out(8);


end if;
end if;
end process;

end Behavioral;

```

FIR:

❖ *RTL Schematic*

 

❖ *VHDL code*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.std_logic_unsigned.ALL;

entity FIR is
  generic (
    coeff_width: integer := 8;
    data_width : integer := 8;
    maximum_vector_length : integer := 19 -- coeff_width + data_width + log2(tap number: 8)
  );
  Port (
    clk : in std_logic;
    rst : in std_logic;
    valid_in : in std_logic;
    x : in std_logic_vector(data_width - 1 downto 0);
    y : out std_logic_vector(maximum_vector_length - 1 downto 0);
    valid_out : out std_logic
  );
end FIR;

architecture Behavioral of FIR is
  component MAC is
    generic (
      coeff_width: integer := 8;
      data_width : integer := 8;
      maximum_vector_length : integer := 19 -- coeff_width + data_width + log2(tap number: 8)
    );
    Port (
      clk : in std_logic;
      rom_out : in std_logic_vector (coeff_width-1 downto 0);
      ram_out : in std_logic_vector(data_width-1 downto 0);
      mac_init, valid_out : in std_logic;
      y_out : out std_logic_vector (maximum_vector_length - 1 downto 0)
    );
  end component;

  component mlab_rom is
    generic (
      coeff_width : integer :=8
    );
    Port ( clk : in STD_LOGIC;
           en : in STD_LOGIC;
           addr : in STD_LOGIC_VECTOR (2 downto 0);
           rom_out : out STD_LOGIC_VECTOR (coeff_width-1 downto 0));
  end component;

  --- width of coefficients (bits)
  --- operation enable
  --- memory address
  --- output data
```

```

component mlab_ram is
  generic (
    data_width : integer :=8                --- width of data (bits)
  );
  port (clk : in std_logic;
        rst : in std_logic;
        we : in std_logic;                  --- memory write enable
        en : in std_logic;                  --- operation enable
        addr : in std_logic_vector(2 downto 0);    -- memory address
        di : in std_logic_vector(data_width-1 downto 0);    -- input data
        ram_out : out std_logic_vector(data_width-1 downto 0));    -- output data
end component;

```

```

component ControlUnit is
  Port (
    clk, rst, valid_in : in std_logic;
    we, mac_init, valid_out : out std_logic;
    rom_address, ram_address : out std_logic_vector(2 downto 0)
  );
end component;

```

```

signal rom_out : std_logic_vector(coeff_width - 1 downto 0);
signal ram_out: std_logic_vector(data_width - 1 downto 0);
signal we, mac_init, mac_init_reg: std_logic := '0';
signal rom_address, ram_address : std_logic_vector(2 downto 0) := (others => '0');
signal x_reg : std_logic_vector(data_width - 1 downto 0);
signal valid_out_reg : std_logic;

```

begin

```

mac_fir: MAC port map (
  clk => clk,
  rom_out => rom_out,
  ram_out => ram_out,
  mac_init => mac_init_reg,
  valid_out => valid_out_reg,
  y_out => y
);

```

```

rom: mlab_rom port map (
  clk => clk,
  en => '1',
  addr => rom_address,
  rom_out => rom_out
);

```

```

ram : mlab_ram port map (

```



```

    clk => clk,
    rst => rst,
    we => we, -- when we = '1' which is set by the control unit when input is valid, ram can start
writing to mac
    en => '1',
    addr => ram_address,
    di => x_reg,
    ram_out => ram_out
);

control_unit: ControlUnit port map (
    clk => clk,
    rst => rst,
    valid_in => valid_in,
    we => we,
    mac_init => mac_init,
    valid_out => valid_out_reg,
    rom_address => rom_address,
    ram_address => ram_address
);

process(clk)
begin
    if rst = '1' then
        x_reg <= (others => '0');
        mac_init_reg <= '0';
    else
        if rising_edge(clk) then
            x_reg <= x;
            mac_init_reg <= mac_init; -- delay mac_init by one cycle for rom and ram to send data to
mac
        end if;
    end if;
end process;

end Behavioral;
```

❖ *Testbench*

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.math_real.all;

entity fir_tb is
end fir_tb;

architecture testbench of fir_tb is
    constant data_width, coeff_width : integer := 8;
    constant maximum_vector_length : integer := 19;

    component fir is
        Port (
            clk : in std_logic;
            rst : in std_logic;
            valid_in : in std_logic;
            x : in std_logic_vector(data_width - 1 downto 0);
            y : out std_logic_vector(maximum_vector_length - 1 downto 0);
            valid_out : out std_logic
        );
    end component;

    --Input Signals
    signal clk: std_logic:='0';
    signal rst: std_logic:='0';
    signal valid_in: std_logic:='0';
    signal x : std_logic_vector(8-1 downto 0):=(others=>'0');
    signal valid_out: std_logic:='0';

    --Output Signals
    signal y : std_logic_vector(19-1 downto 0):=(others=>'0');

    --Clock
    constant CLK_PERIOD : time := 10ns;

begin

    clk_process: process
    begin
        clk <= '0';
        wait for CLK_PERIOD/2;
        clk <= '1';
        wait for CLK_PERIOD/2;
```

```
end process;
```

```
UUT: fir port map (  
    clk => clk,  
    rst => rst,  
    valid_in => valid_in,  
    x => x ,  
    y => y,  
    valid_out => valid_out  
);
```

```
TEST:
```

```
process  
begin  
    rst <= '1';  
    valid_in <= '1';  
    x <= std_logic_vector(to_unsigned(208, 8));  
    wait for CLK_PERIOD/4;  
    rst <= '0';  
    wait for 3*CLK_PERIOD/4;  
    valid_in <= '0';  
    wait for 7*CLK_PERIOD;  
  
    valid_in <= '1';  
    x <= std_logic_vector(to_unsigned(231, 8));  
    wait for CLK_PERIOD;  
    valid_in <= '0';  
    wait for 7*CLK_PERIOD;  
  
    valid_in <= '1';  
    x <= std_logic_vector(to_unsigned(32, 8));  
    wait for CLK_PERIOD;  
    valid_in <= '0';  
    wait for 7*CLK_PERIOD;  
  
    valid_in <= '1';  
    x <= std_logic_vector(to_unsigned(233, 8));  
    wait for CLK_PERIOD;  
    valid_in <= '0';  
    wait for 7*CLK_PERIOD;  
  
    valid_in <= '1';  
    x <= std_logic_vector(to_unsigned(161, 8));  
    wait for CLK_PERIOD;  
    valid_in <= '0';  
    wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(24, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(71, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(140, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(245, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(247, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(40, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(248, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```
valid_in <= '1';  
x <= std_logic_vector(to_unsigned(245, 8));  
wait for CLK_PERIOD;  
valid_in <= '0';  
wait for 7*CLK_PERIOD;
```

```

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(124, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(204, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(36, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(107, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(234, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;

    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(202, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;


    valid_in <= '1';
    x <= std_logic_vector(to_unsigned(245, 8));
    wait for CLK_PERIOD;
    valid_in <= '0';
    wait for 7*CLK_PERIOD;
wait;

end process;

end testbench;

```

 ❖ Post-Implementation Functional Simulation



Το FIR φίλτρο λειτουργεί στο στάδιο Post-Implementation κατάλληλα, χωρίς undefined ή high impedance σήματα. Η έξοδος y παράγεται ακριβώς κάθε 8 κύκλους ρολογιού ως η συνέλιξη των εισόδων x με τους συντελεστές h στη ROM, ενώ ενεργοποιείται το σήμα valid_out, στον ίδιο κύκλο ρολογιού που το y λαμβάνει το τελικό αποτέλεσμα για τη νέα είσοδο.

❖ Resources και Critical Path

Για την υλοποίηση του φίλτρου FIR στο FPGA, χρειάζονται συνολικά **88 Look Up Tables και 142 Flip Flops**. Καθώς το φίλτρο είναι μικρής κλίμακας, δεν χρειάστηκαν DSP slices ή BRAM/URAM blocks.

Name	Constraints	Status	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	Methodology	RQA Score	QoR Suggestions	LUT	FF	BRAM	URAM	DSP
✓ synth_1	constrs_1	synth_design Complete!												88	142	0	0	0
✓ impl_1	constrs_1	route_design Complete!	NA	NA	NA	NA		NA	18.080	0	142 CW			88	142	0	0	0

Το κρίσιμο μονοπάτι έχει καθυστέρηση **7.577nS**. Αποτελεί το μονοπάτι από το clock input pin του rom_out[2] στο data input pin του καταχωρητή feedback_reg[17].

Name	Slack	Levels	High Fanout	From	To	Total ...	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	10	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[17]/D	7.577	2.686	4.891	∞	
Path 2	∞	10	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[18]/D	7.321	2.597	4.724	∞	
Path 3	∞	10	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[16]/D	7.306	2.571	4.735	∞	
Path 4	∞	9	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[9]/D	7.175	2.835	4.340	∞	
Path 5	∞	9	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[8]/D	7.140	2.718	4.422	∞	
Path 6	∞	9	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[10]/D	6.886	2.718	4.168	∞	
Path 7	∞	9	20	rom/rom_out_reg[2]/C	mac_fir/feedback_reg[11]/D	6.631	2.800	3.831	∞	

Από το κρίσιμο μονοπάτι, η μέγιστη συχνότητα λειτουργίας του FPGA, υπολογίζεται ως:

$$f_{max} = \frac{1}{t_{delay}} = 131.98MHz$$

Ωστόσο, για την ευσταθή λειτουργία του κυκλώματος, θα επιλεγόταν μικρότερη συχνότητα από τη μέγιστη. Τα timing delays μπορεί να διαφέρουν λόγω των διακυμάνσεων PVT αλλά και για να περιοριστεί η κατανάλωση ισχύος, μένοντας εντός των προδιαγραφών λειτουργίας.